

2-Stage Operational Amplifier Design

Vinay Pandey
Roll no.-244102115

1 Requirements

Schematic and Specification

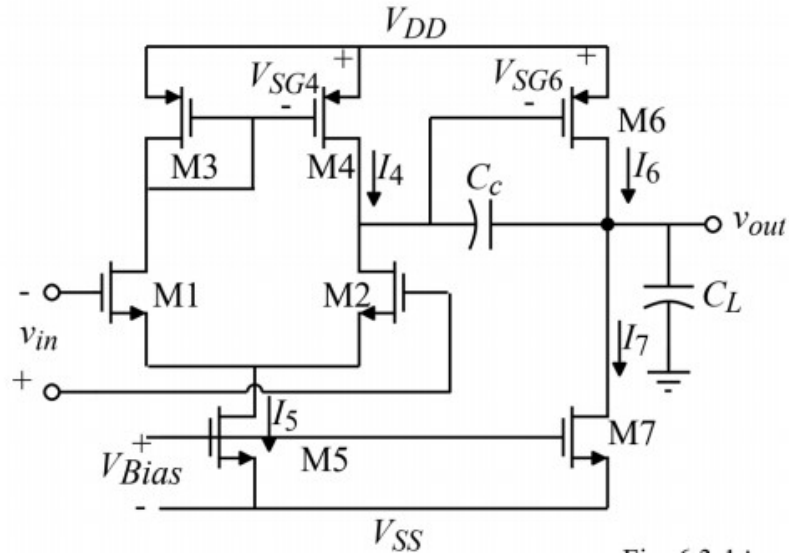


Figure 1: Two-stage CMOS Op-Amp schematic with compensation capacitor C_c and load capacitor C_L .

As shown in Fig. 1, the circuit consists of input transistors M_1, M_2 , current mirror load M_3, M_4 , biasing transistor M_5 , output stage M_6 , and current sink M_7 .

Assume the channel length is to be $0.5 \mu m$, load capacitor is $C_L = 10 \text{ pF}$.

| | |
|---|---|
| $A_v > 3000 \text{ V/V}$ | $V_{DD} = 0.9 \text{ V}, V_{SS} = -0.9 \text{ V}$ |
| $GB = 10 \text{ MHz}$ | $SR > 12 \text{ V}/\mu s$ |
| Phase margin = 60° | $-0.5 \text{ V} < V_{out} < 0.5 \text{ V}$ |
| $ICMR = -0.5 \text{ V to } 0.5 \text{ V}$ | $P_{diss} \leq 3 \text{ mW}$ |

2 Calculate Kn, Kp from library 180nm

$$V_{TN} = 0.393; \quad V_{TP} = -0.4; \quad \lambda_N = 0.07; \quad \lambda_P = 0.07$$

$$K_n = \mu_n \times C_{ox} = 280.575 \text{ cm}^2/\text{Vs} \times \left(\frac{\varepsilon_{ox}}{T_{ox}} \right)$$

$$C_{ox} = \frac{3.9 \times 8.854 \times 10^{-12}}{4.1 \times 10^{-9}} \text{ F/m}^2$$

$$\Rightarrow C_{ox} = 8.422 \times 10^{-3} \text{ F/m}^2 = 0.8422 \mu\text{As}/V(\text{cm})^2$$

$$\Rightarrow K_n = 280.575 \text{ cm}^2/\text{Vs} \times 0.8422 \mu\text{As}/V(\text{cm})^2 = 236.3 \mu\text{A}/V^2$$

$$K_p = \mu_p \times C_{ox} = 116.169 \text{ cm}^2/\text{Vs} \times \left(\frac{\varepsilon_{ox}}{T_{ox}} \right)$$

$$\Rightarrow K_p = 116.169 \text{ cm}^2/\text{Vs} \times 0.8422 \mu\text{As}/V(\text{cm})^2 = 97.837 \mu\text{A}/V^2$$

3 Transistor Sizing Calculations

3.1 Calculation W1, W2

$$g_{m1} = GB \times C_c \times 2\pi = 10 \text{ MHz} \times 5 \text{ pF} \times 2\pi = \mathbf{314 \mu S}$$

$$\Rightarrow \frac{W_1}{L_1} = \frac{(g_{m1})^2}{2K_n I_D} = \frac{(314 \mu S)^2}{236.3 \mu\text{A}/V^2 \times 60 \mu\text{A} \times 1.5} = 6.954$$

$$\Rightarrow W_1 = W_2 = 6.954 \times 0.5 \mu m = \boxed{3.477 \mu m}$$

3.2 Calculation W3, W4

- With L of PMOS and NMOS are 0.5 μm

$$C_c > 0.22C_L = 0.22 \times 10 \text{ pF} = 2.2 \text{ pF} \Rightarrow \text{Choose } C_c = \mathbf{5 \text{ pF}}$$

$$I_S = SR \times C_c = 12 \times 10^6 \times 5 \times 10^{-12} = \mathbf{60 \mu A}$$

$$\frac{W_3}{L_3} = \frac{I_S}{K_p(V_{DD} - V_{CM(\min)} - |V_{T3}|)^2} = \frac{60 \mu\text{A}}{97.837 \mu\text{A}/V^2 \times (0.9 - 0.5 - 0.4 + 0.393)^2} = 3.97$$

$$\Rightarrow W_3 = W_4 = 3.97 \times 0.5 \mu m = \boxed{1.985 \mu m}$$

3.3 Calculation W5

$$\begin{aligned}
 V_{DSS} &= V_{CM(\min)} - \left(\sqrt{\frac{I_5}{K_n(W_1/L_1)}} - V_{T1} \right) - V_{SS} \\
 &= -0.5 - \left(\sqrt{\frac{60 \mu A}{236.3 \mu A/V^2 \times 6.954}} - 0.393 \right) + 0.9 = -0.18480 V \\
 \Rightarrow \frac{W_5}{L_5} &= \frac{2I_5}{K_n(V_{DSS})^2} = \frac{2 \times 60 \mu A}{236.3 \mu A/V^2 \times (-0.18480)^2} = 14.986 \\
 \Rightarrow W_5 &= 14.986 \times 0.5 \mu m = \boxed{7.493 \mu m}
 \end{aligned}$$

3.4 Calculation W6

$$\text{Phase margin} = 60^\circ \Rightarrow g_{m6} = 10g_{m1} = 10 \times 314 \mu S = 3140 \mu S$$

$$\begin{aligned}
 g_{m4} &= \sqrt{2K_p(W_4/L_4)I_4}, \quad I_4 = 0.5I_S \\
 \Rightarrow g_{m4} &= \sqrt{2 \times 97.837 \mu A/V^2 \times 3.97 \times 60 \mu A} = 152.66 \mu S \\
 \frac{W_6}{L_6} &= \frac{W_4}{L_4} \times \frac{g_{m6}}{g_{m4}} = 3.97 \times \frac{3140 \mu S}{152.66 \mu S} = 81.66 \\
 \Rightarrow W_6 &= 81.66 \times 0.5 \mu m = \boxed{40.83 \mu m}
 \end{aligned}$$

3.5 Calculation W7, Power Dissipation and Voltage Gain

$$I_6 = \frac{(g_{m6})^2}{2K_p(W_6/L_6)} = \frac{(3140 \mu S)^2}{2 \times 97.837 \mu A/V^2 \times 81.66} = 617 \mu A$$

Choose $I_C = 315 \mu A$, reduce I_6 to increase A_v

$$P_{diss} = (V_{DD} + |V_{SS}|)(I_5 + I_6) = 1.8 \times (60 \mu A + 315 \mu A) = 0.675 mW < 3 mW$$

$$A_v = \frac{2g_{m1}g_{m6}}{I_5((\lambda_2 + \lambda_6)(\lambda_6 + \lambda_7))} = \frac{2 \times 314 \mu S \times 3140 \mu S}{0.12 \times 315 \mu A \times 60 \mu A} = \boxed{5323 V/V}$$

4 Calculate V_{bias} , $V_{\text{out(max)}}$, and $V_{\text{out(min)}}$

$$I_{SS} = 0.5K_n \left(\frac{W_5}{L_5} \right) (|V_{GSS}| - V_{TN})^2$$

$$\Rightarrow 60 \mu A = 0.5 \times 236.3 \mu A/V^2 \times 14.986 \times (|-0.9 - V_{\text{bias}} - 0.393|)^2$$

$$|-0.9 - V_{\text{bias}}| = 0.577 V$$


$$\Rightarrow V_{\text{bias}} = \boxed{-0.323 V}$$

$$V_{\text{out(max)}} = V_{DD} - V_{DS6(\text{SAT})} = 0.9 - \sqrt{\frac{2I_6}{K_p(W_6/L_6)}} = 0.9 - 0.28 = \boxed{0.62 V}$$

$$V_{\text{out(min)}} = V_{SS} + V_{DS7(\text{SAT})} = -0.9 + \sqrt{\frac{2I_6}{K_n(W_7/L_7)}} = -0.9 + 0.18 = \boxed{-0.72 V}$$


❖ Results

- LTSPICE schematic:

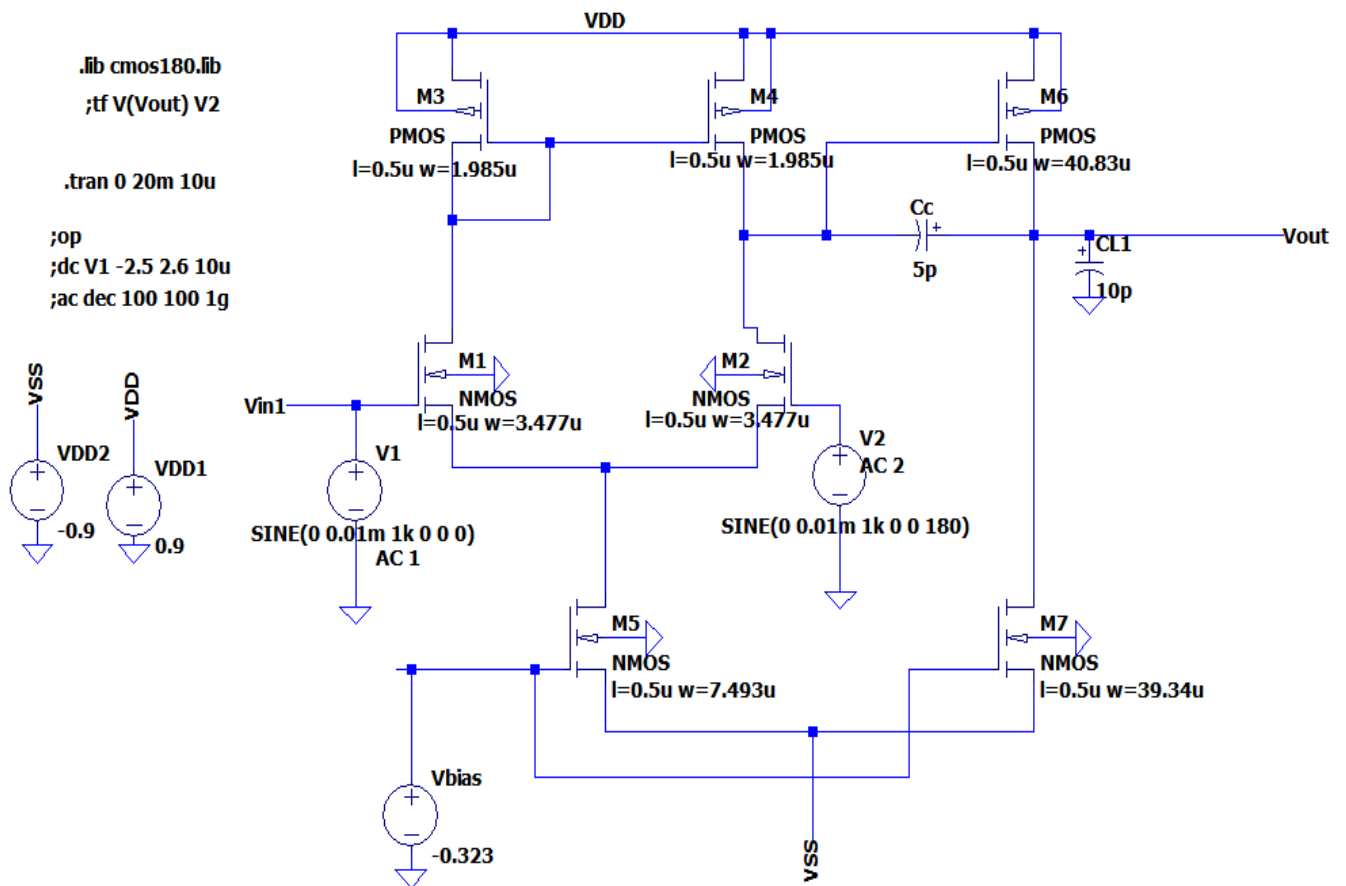


- Simulation of A_v : V_{pp} of V_{in} is 10uV, V_{pp} of V_{out} is 56.3mV
 
$$A_v = 56.3\text{mV} / 10\text{uV} = 5630 \text{ V/V}$$




- **Simulation of Gain Bandwidth and Phase Margin:**

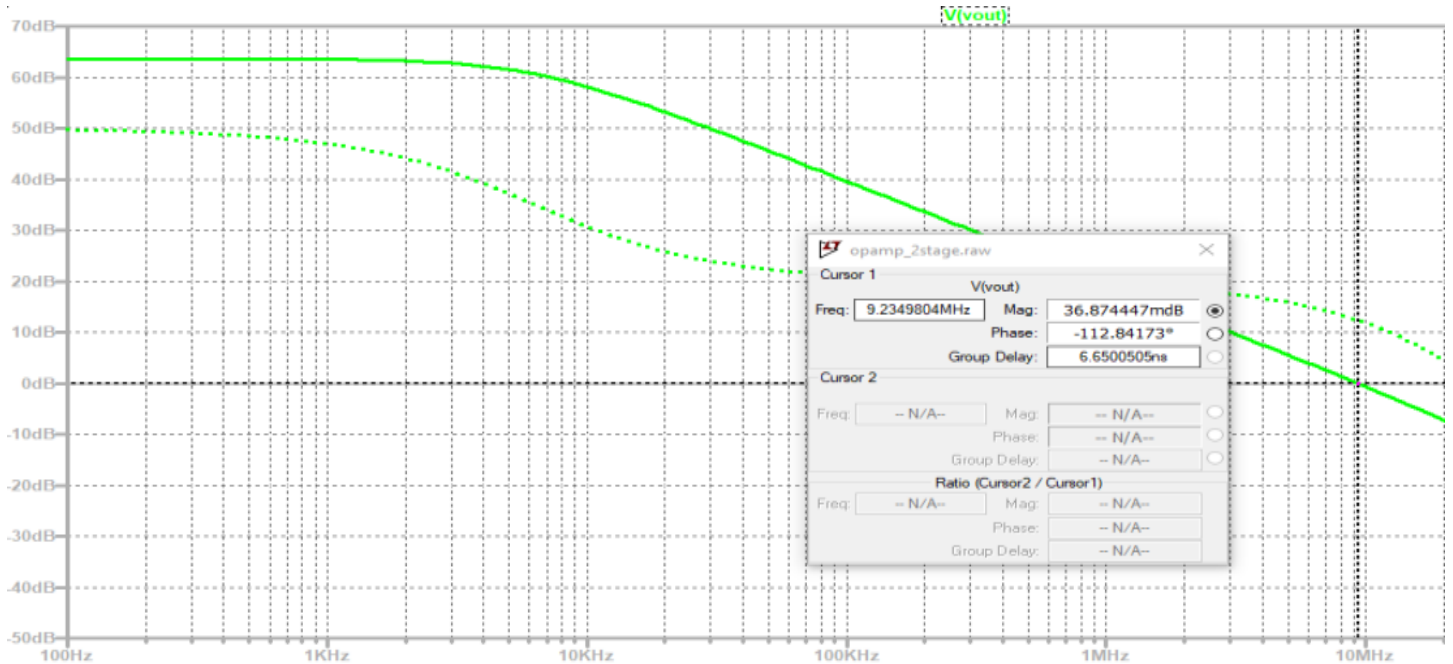At 0dB have GB = 9.23MHz and PM = 180 - 112 = 68 degree




- **Simulation of ICMR:**

 Connect Vout with Vin(-) and simulate in DC mode has ICMR: -0.081V -> 0.333V




- **Simulation of Vout range:**

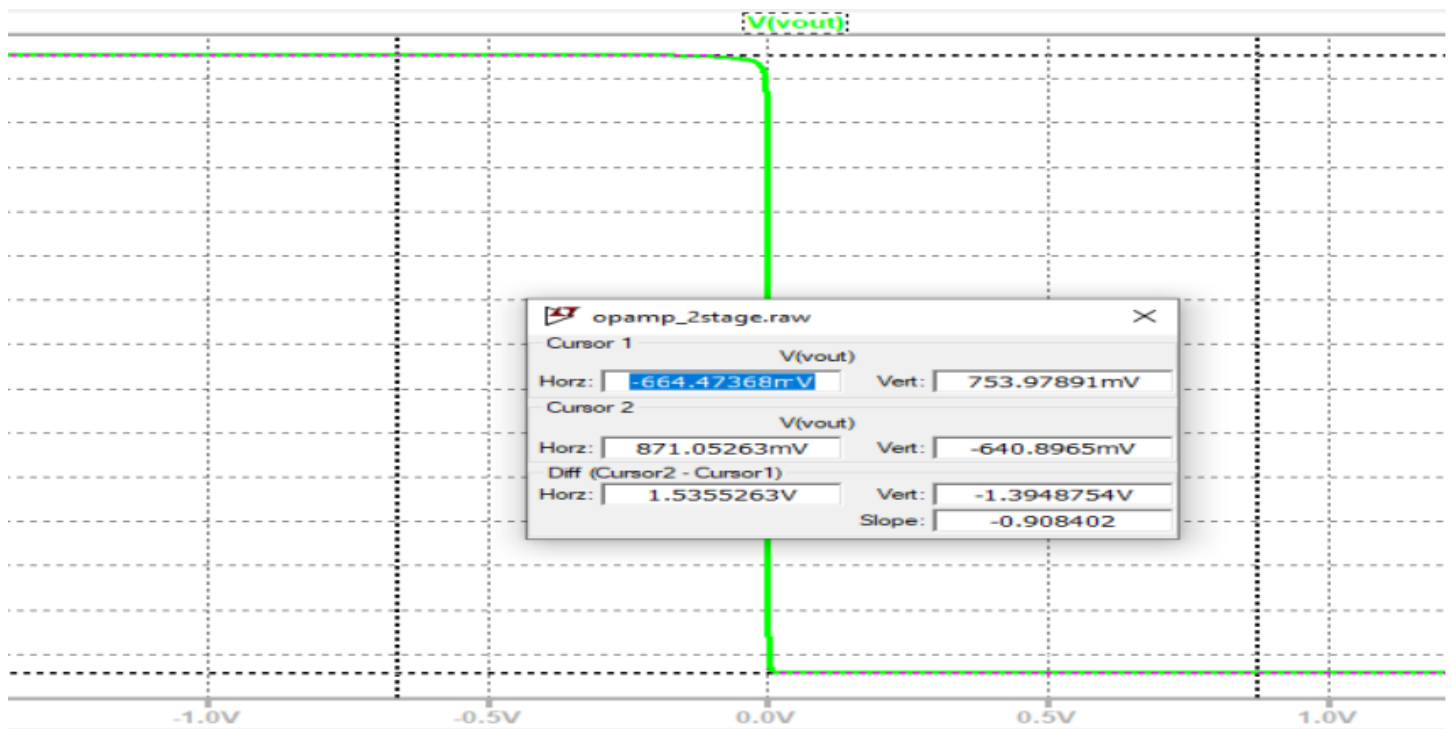simulate with DC mode has Vout range: -0.64V -> 0.753V



- **Simulation of Slew Rate:**

 

- Simulation of Power Dissipation

$$P_{\text{diss}} = (V_{\text{DD}} + |V_{\text{SS}}|) \cdot I_{\text{SS}} = (0.9\text{V} + 0.9\text{V}) \cdot 95.735\mu\text{A} = 0.1723\text{mW}$$

```

Id(M4) : 9.81037e-013 device_current
Is(M4) : -3.02648e-005 device_current
Id(M7) : 0.000620031 device_current
Ig(M7) : 0 device_current
Ib(M7) : 0.586354 device_current
Is(M7) : -0.586975 device_current
Id(M5) : 9.57356e-005 device_current
Ig(M5) : 0 device_current
Ib(M5) : 0.586372 device_current
Is(M5) : -0.586468 device_current
Id(M2) : 3.02648e-005 device_current
Ig(M2) : 0 device_current
Ib(M2) : 1.7603e-005 device_current
Is(M2) : -4.78678e-005 device_current

```

- Comparison

| Value | Requirement | Calculation | Simulation |
|------------------------|--|--|--|
| A_v | $> 3000 \text{ V/V}$ | 5323 V/V | 5630 V/V |
| GB | 10 MHz | 10 MHz | 9.23 MHz |
| $V_{\text{out range}}$ | $-0.5\text{V} \rightarrow 0.5\text{V}$ | $-0.72\text{V} \rightarrow 0.62\text{V}$ | $-0.64\text{V} \rightarrow 0.753\text{V}$ |
| ICMR | $-0.5\text{V} \rightarrow 0.5\text{V}$ | $-0.5\text{V} \rightarrow 0.5\text{V}$ | $-0.081\text{V} \rightarrow 0.333\text{V}$ |
| P_{diss} | $\leq 3 \text{ mW}$ | 0.675 mW | 0.1723 mW |
| Phase Margin | 60° | 60° | 68° |
| Slew Rate | $> 12 \text{ V}/\mu\text{s}$ | $12 \text{ V}/\mu\text{s}$ | $0.22 \text{ mV}/\mu\text{s}$ |